 


15-251

Great Theoretical Ideas in Computer Science


Lecture 12: Boolean Circuits



October 6th, 2015

Where we are, where we are going

Monday	Tuesday	Wednesday	Thursday	Friday
<u>Aug 29</u>	<u>Aug 30</u> Introduction	<u>Aug 31</u> On proofs	<u>Sep 1</u> Combinatorial Games	<u>Sep 2</u>
<u>Sep 5</u>	<u>Sep 6</u> Finite Automata	<u>Sep 7</u> hw1 w.s.	<u>Sep 8</u> Turing Machines	<u>Sep 9</u>
<u>Sep 12</u>	<u>Sep 13</u> Uncountability	<u>Sep 14</u> hw2 w.s.	<u>Sep 15</u> Undecidability	<u>Sep 16</u>
<u>Sep 19</u>	<u>Sep 20</u> Intro to Complexity 1	<u>Sep 21</u> hw3 w.s.	<u>Sep 22</u> Intro to Complexity 2	<u>Sep 23</u>
<u>Sep 26</u>	<u>Sep 27</u> Graphs 1	<u>Sep 28</u> hw4 w.s.	<u>Sep 29</u> Graphs 2	<u>Sep 30</u>
<u>Oct 3</u>	<u>Oct 4</u> Graphs 3	<u>Oct 5</u> Midterm 1	<u>Oct 6</u> Boolean Circuits	<u>Oct 7</u>
<u>Oct 10</u>	<u>Oct 11</u> NP-completeness 1	<u>Oct 12</u> hw5 w.s.	<u>Oct 13</u> NP-completeness 2	<u>Oct 14</u>

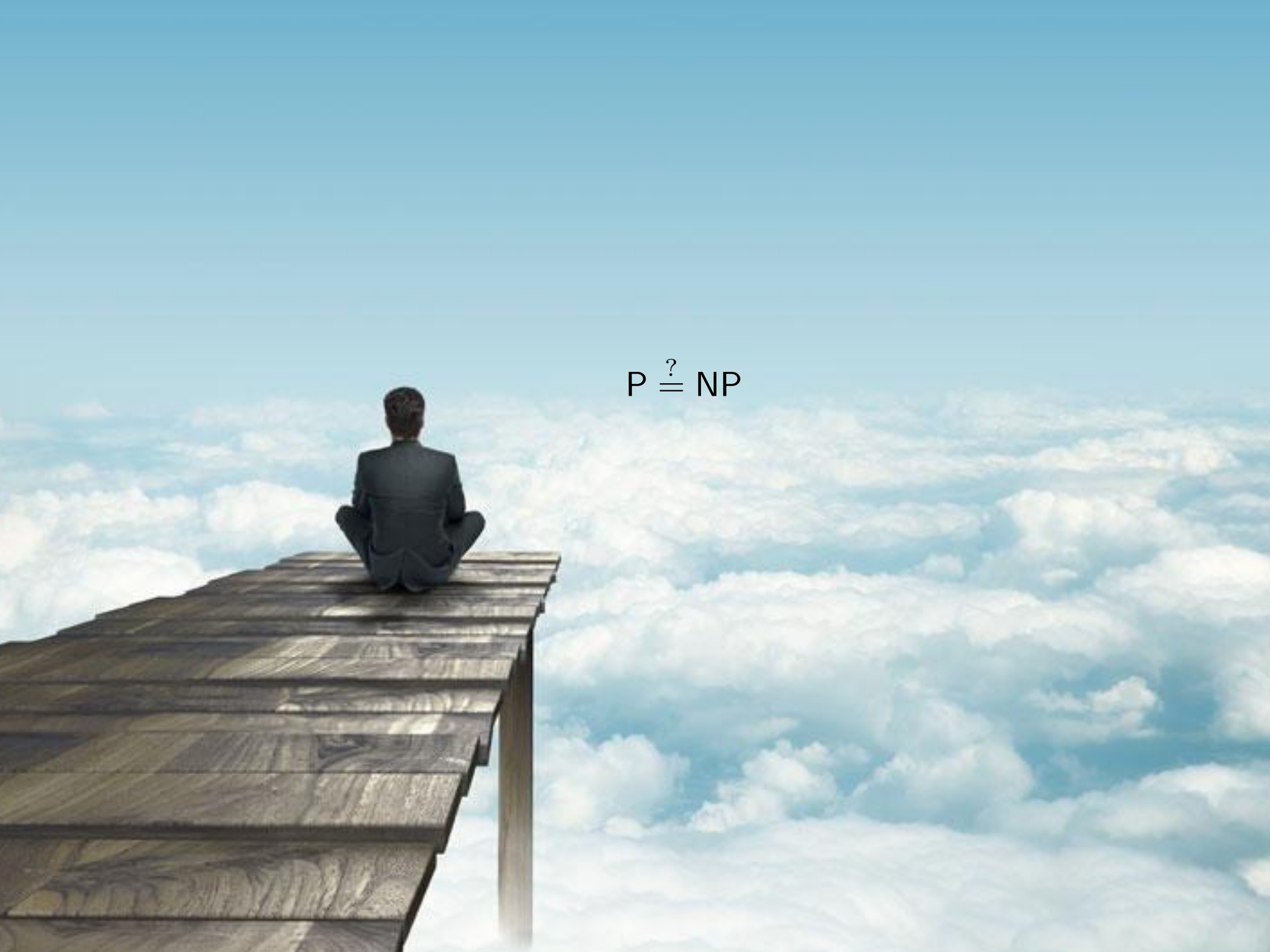A person in a dark suit is sitting cross-legged on a long, narrow wooden plank that extends from the bottom left towards the center of the frame. The plank is supported by a single vertical post. Below the plank is a vast, dense layer of white, fluffy clouds that stretch to the horizon. The sky above is a clear, light blue. The overall scene conveys a sense of contemplation and vastness.

$P \stackrel{?}{=} NP$

Computational complexity of a problem

How to show an **upper bound** on the intrinsic complexity?

> Give an algorithm that solves the problem.

How to show a **lower bound** on the intrinsic complexity?

> Argue against all possible algorithms that solve the problem.

The dream: Get a matching upper and lower bound.

What is P ?

P

The set of languages that can be decided in $O(n^k)$ steps for some constant k .

The theoretical divide between **efficient** and **inefficient**:

$L \in P \longrightarrow$ **efficiently** solvable.


$L \notin P \longrightarrow$ **not** efficiently solvable.

What is NP ?

EXP

The set of languages that can be decided in $O(2^{n^k})$ steps for some constant $k > 0$.

DECIDABLE LANGUAGES

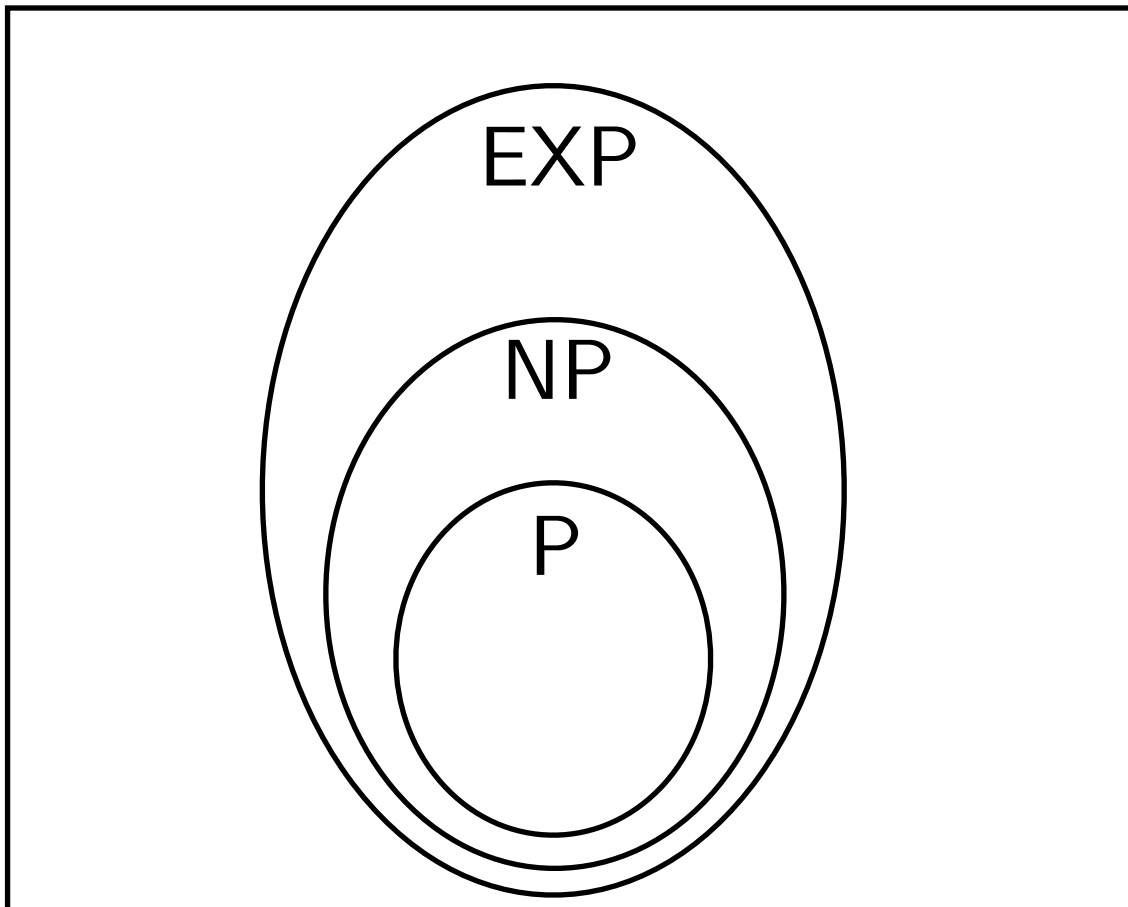


NP:

A class between

P and EXP.

What is NP ?

 

$$P \stackrel{?}{=} NP$$

asks whether these two sets are equal.

How would you show $P = NP$?

- > Show that every problem in NP can be solved in poly-time.

How would you show $P \neq NP$?

- > Show that there is a problem in NP which cannot be solved in poly-time.

You have to argue against all possible poly-time TMs.

Boolean Circuits

Some preliminary questions

What is a Boolean circuit?

- It is a computational model for computing decision problems (or computational problems).


We already have TMs. Why Boolean circuits?

- The definition is simpler.
- Easier to understand, usually easier to reason about.
- Boolean circuits can efficiently simulate TMs.
(efficient decider TM \implies efficient/small circuits.)
- Circuits are good models to study *parallel computation*.
- Real computers are built with digital circuits.

Sounds AWESOME!
So why didn't we just learn about circuits first?

There is a small catch.

 An algorithm is a **finite** answer
to **infinite** number of questions.



Stephen Kleene
(1909 - 1994)

Sounds AWESOME!
So why didn't we just learn about circuits first?

There is a small catch.

Circuits are an **infinite** answer
to **infinite** number of questions.



Anil Ada
(???? - 2077)

Dividing a problem according to length of input

$$\Sigma = \{0, 1\}$$

$$L \subseteq \{0, 1\}^*$$

$$L_n = \{w \in L : |w| = n\}$$

$$L = L_0 \cup L_1 \cup L_2 \cup \dots$$

$$f : \{0, 1\}^* \rightarrow \{0, 1\}$$

$\{0, 1\}^n$ = all strings of length n

$$f^n : \{0, 1\}^n \rightarrow \{0, 1\}$$


for $x \in \{0, 1\}^n$,

$$f^n(x) = f(x)$$


$$f = (f^0, f^1, f^2, \dots)$$

Dividing a problem according to length of input

 A TM is a finite object (finite number of states)
but can handle any input length.



 Imagine a model where we allow the TM to grow
with input length.



Dividing a problem according to length of input

So one machine does not compute L .

You use a **family** of machines:

$$(M_0, M_1, M_2, \dots)$$

(Imagine having a different Python function for each input length.)




Is this a reasonable/realistic model of computation?!?

Boolean circuits work this way.


Need a separate circuit for each input length.

Boolean Circuit Definition


Picture of a circuit

 

Picture of a circuit

 


Picture of a circuit

 

binary OR gate




binary AND gate

 

unary NOT gate






 


input gate

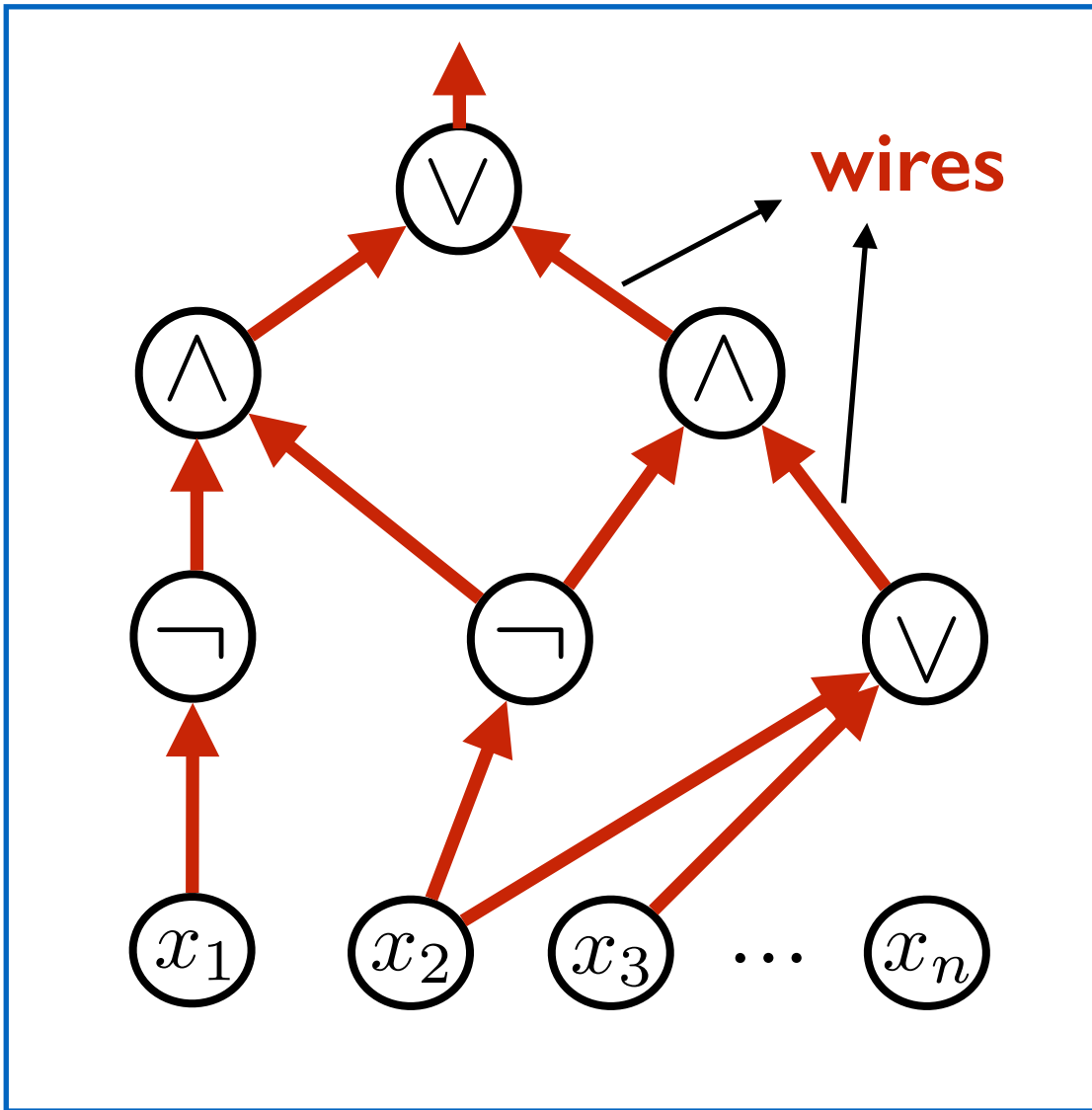


output gate

Picture of a circuit

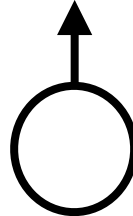

-  binary OR gate
-  binary AND gate
-  unary NOT gate
-  input gate
-  output gate

Picture of a circuit


 


No feedback loops
allowed!

It is a directed acyclic
graph.

Information flows from input gates to the output gate.



Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?



Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?



Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?


Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?

Picture of a circuit


 


- \vee binary OR gate
- \wedge binary AND gate
- \neg unary NOT gate
- x_i input gate
- \uparrow output gate

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?



Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?



Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?


Picture of a circuit

  

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?

Picture of a circuit


 


- \vee binary OR gate
- \wedge binary AND gate
- \neg unary NOT gate
- x_i input gate
- \uparrow output gate

Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?

Picture of a circuit

  


Computes a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$.

So how does it compute $f(x_1, x_2, \dots, x_n)$?


Poll: What does this circuit compute ?

 (sometimes circuits are drawn upside down)




Poll: What does this circuit compute ?

 (sometimes circuits are drawn upside down)



Poll: What does this circuit compute ?

 (sometimes circuits are drawn upside down)



How does a circuit **decide/compute** a language?

How do we measure the **complexity** of a circuit?

How can a circuit compute a language?


A circuit has a fixed number of inputs.

How can we compute/decide a decision problem

$f : \{0, 1\}^* \rightarrow \{0, 1\}$ with circuits?

$f = (f^0, f^1, f^2, \dots)$ where $f^n : \{0, 1\}^n \rightarrow \{0, 1\}$

 Construct a circuit for each input length.



A **circuit family** C is a collection of circuits (C_0, C_1, C_2, \dots) where each C_n takes n input variables.

How can a circuit compute a language?

We say that a circuit family $C = (C_0, C_1, C_2, \dots)$

decides/computes $f : \{0, 1\}^* \rightarrow \{0, 1\}$

if C_n computes f^n for every n .

Circuit size and complexity

Definition: [size of a circuit]

The **size of a circuit** is the total number of gates (counting the input variables as gates too) in the circuit.

Definition: [size of a circuit family]

The **size of a circuit family** $C = (C_0, C_1, C_2, \dots)$ is a function $s(\cdot)$ such that $s(n) = \text{size of } C_n$.

Definition: [circuit complexity]

The **circuit complexity** of a decision problem is the size of the minimal circuit family that decides it.

(This is the intrinsic complexity with respect to circuit size)

Poll

Let $f : \{0, 1\}^* \rightarrow \{0, 1\}$ be the parity decision problem.

$$f(x) = x_1 + \dots + x_n \pmod{2} \quad (\text{where } n = |x|)$$

$$f(x) = x_1 \oplus \dots \oplus x_n$$

What is the circuit complexity of this function?

Choose the tightest one:

$$O(n)$$

$$O(2^n)$$

$$O(n^2)$$


$$O(2^{2^n})$$

$$O(n^{2.5})$$

None of the above.

Beats me.

Poll

 

$$s(n) = 2s(n/2) + 5$$

$$s(1) = 1$$

$$\implies s(n) = O(n).$$

The Big Picture Regarding Boolean Circuits

The big picture

Computability with respect to circuits

Theorem: Any decision problem $f : \{0, 1\}^* \rightarrow \{0, 1\}$ can be computed by a circuit family of size $O(2^n)$.

The big picture

Limits of efficient computability with respect to circuits

Theorem: There exists a decision problem such that any circuit family computing it must have size at least $2^n / 4n$.

In fact, most decision problems require exponential size.

The big picture

Circuits can efficiently “simulate” TMs

Theorem: Let $f : \{0, 1\}^* \rightarrow \{0, 1\}$ be a decision problem which can be decided in time $O(T(n))$.


Then it can be computed by a circuit family of size $O(T(n)^2)$.

poly-time TM \implies poly-size circuits

no poly-size circuits \implies no poly-time TM

The big picture

Circuits can efficiently “simulate” TMs

 

To show $P \neq NP$:

Find h in NP whose circuit complexity is more than $\text{poly}(n)$.

The big picture

So we can just work with circuits instead


This is awesome in 2 ways:

1. **Circuits:** clean and simple definition of computation.
“Just” a composition of **AND**, **OR**, **NOT** gates.

2. Restrict the circuit.
Make it less powerful.

e.g. (i) restrict *depth*

(ii) restrict types of gates

 

The big picture

So we can just work with circuits instead

Exciting progress was made in the 1980s.

People thought $P \neq NP$ would be proved soon.

Alas...

After 60 years of research,
best lower bound on circuit size for an explicit function:

$5n$ – peanuts

The big picture

Theorem: Any decision problem $f : \{0, 1\}^* \rightarrow \{0, 1\}$ can be computed by a circuit family of size $O(2^n)$.

Theorem: There exists a decision problem such that any circuit family computing it must have size at least $2^n / 4n$.

Theorem: Let $f : \{0, 1\}^* \rightarrow \{0, 1\}$ be a decision problem which can be decided in time $O(T(n))$. Then it can be computed by a circuit family of size $O(T(n)^2)$.

Theorem 1: Max circuit size of a function

Theorem: Any decision problem $f : \{0, 1\}^* \rightarrow \{0, 1\}$ can be computed by a circuit family of size $O(2^n)$.

Proof:

Goal:

construct a circuit of size $O(2^n)$ for $f^n : \{0, 1\}^n \rightarrow \{0, 1\}$.

Observation:

$$f^n(x_1, x_2, \dots, x_n) = (x_1 \wedge f^n(1, x_2, \dots, x_n)) \vee (\neg x_1 \wedge f^n(0, x_2, \dots, x_n))$$

Theorem 1: Max circuit size of a function

Theorem: Any decision problem $f : \{0, 1\}^* \rightarrow \{0, 1\}$ can be computed by a circuit family of size $O(2^n)$.

Proof:

Goal:

construct a circuit of size $O(2^n)$ for $f^n : \{0, 1\}^n \rightarrow \{0, 1\}$.

Observation:

$$f^n(x_1, x_2, \dots, x_n) = \left(\cancel{x_1} \wedge f^n(1, x_2, \dots, x_n) \right) \vee \left(\cancel{\neg x_1} \wedge f^n(0, x_2, \dots, x_n) \right)$$

if $x_1 = 1$

0 0

Theorem 1: Max circuit size of a function

Theorem: Any decision problem $f : \{0, 1\}^* \rightarrow \{0, 1\}$ can be computed by a circuit family of size $O(2^n)$.

Proof:

Goal:

construct a circuit of size $O(2^n)$ for $f^n : \{0, 1\}^n \rightarrow \{0, 1\}$.


Observation:

$$f^n(x_1, x_2, \dots, x_n) = \overset{0}{\cancel{(x_1 \wedge f^n(1, x_2, \dots, x_n))}} \vee \overset{0}{\cancel{(\neg x_1 \wedge f^n(0, x_2, \dots, x_n))}}$$

if $x_1 = 0$

Theorem 1: Max circuit size of a function

Proof (continued):

 

$s(n)$ = max size of a circuit computing n -variable function

$$s(n) \leq 2s(n-1) + 5, \quad s(1) \leq 3 \implies s(n) = O(2^n) \quad \square$$

Poll

How many different functions $f : \{0, 1\}^n \rightarrow \{0, 1\}$ are there?

- n
- $2n$
- n^2
- 2^n
- 2^{2^n}
- none of the above
- beats me

Theorem 2: Some functions are hard

Theorem: There exists a decision problem such that any circuit family computing it must have size at least $2^n / 5n$.

Proof:

Want to show: there is a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$ that cannot be computed by a circuit of size $< 2^n / 5n$.

Observation: # possible functions is 2^{2^n} .

Claim 1: # circuits of size at most s is $\leq 2^{5s \log s}$.

Claim 2: For $s \leq 2^n / 5n$, $2^{5s \log s} < 2^{2^n}$.

circuits $<$ # functions

Theorem 2: Some functions are hard

Theorem: There exists a decision problem such that any circuit family computing it must have size at least $2^n / 5n$.

Proof:

Want to show: there is a function $f : \{0, 1\}^n \rightarrow \{0, 1\}$ that cannot be computed by a circuit of size $< 2^n / 5n$.

Observation: # possible functions is 2^{2^n} .

Claim 1: # circuits of size at most s is $\leq 2^{5s \log s}$.

Claim 2: For $s \leq 2^n / 5n$, $2^{5s \log s} < 2^{2^n}$.

We are done once we prove Claim 1. (Claim 2 is easy/uninteresting.)

Theorem 2: Some functions are hard

Proof (continued):

Claim I: # circuits of size at most s is $\leq 2^{5s \log s}$.

Proof of claim:

Recall $|A| \leq |B|$ iff $B \rightarrow A$.

Let $A = \{\text{circuits of size at most } s\}$

$$B = \{0, 1\}^{5s \log s} \quad |B| = 2^{5s \log s}$$

To show $B \rightarrow A$:

encode a circuit with a binary string of length $5s \log s$.

(just like the CS method)

Theorem 2: Some functions are hard

Proof (continued):

Claim I: # circuits of size at most s is $\leq 2^{5s \log s}$.

Proof of claim (continued):

Encoding a circuit with a binary string of length $5s \log s$:

Number the gates: $1, 2, 3, 4, \dots, s$

For each gate in the circuit, write down:

- type of the gate (3 bits)
- from which gates the inputs are coming from (2 log s bits)

Total: $s(3 + 2 \log s)$ bits


$(3s + 2s \log s)$ bits $\leq (5s \log s)$ bits



Theorem 2: Some functions are hard

That was due to Claude Shannon (1949).

Father of *Information Theory*.

 

Claude Shannon
(1916 - 2001)

A **non-constructive** argument.

In fact, it is easy to show that most functions require exponential size circuits.


Theorem 3: Circuits can simulate TMs


Theorem: Let $f : \{0, 1\}^* \rightarrow \{0, 1\}$ be a decision problem which can be decided in time $O(T(n))$. Then it can be computed by a circuit family of size $O(T(n)^2)$.

How can you prove such a theorem?

If you like a challenge, try to prove it yourself.

If you don't like a challenge, but still curious, see the course notes for a sketch of the proof.

If you don't like a challenge, and are not curious,
 you can ignore the proof.

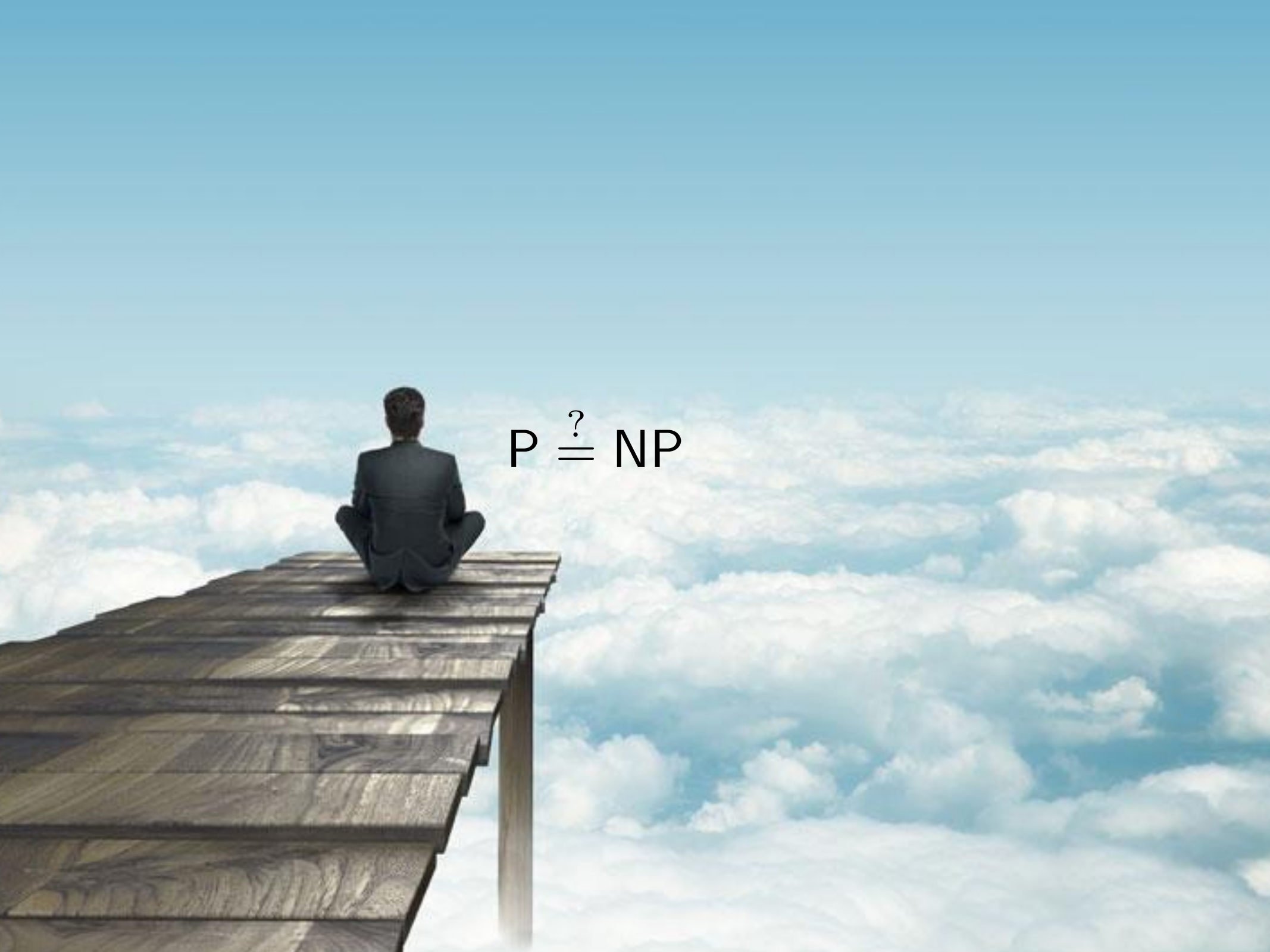A person in a dark suit is sitting cross-legged on a long, narrow wooden pier that extends from the bottom left towards the center of the frame. The pier is made of dark, weathered wooden planks. Below the pier is a vast, dense layer of white, fluffy clouds that stretch across the entire width of the image. Above the clouds is a clear, light blue sky. The overall scene is surreal and contemplative.

$P \stackrel{?}{=} NP$